

Circuits

Fill in the missing words

loop

unbroken

current

route

negative

positive

electrical

A circuit is a route that allows electrical current to flow through it.

Electricity always travels from the negative to the positive.

A circuit will only work if it is unbroken. This means it must make a complete loop, otherwise the electrical current cannot flow.

Draw arrows on the diagram to show which way the electricity is flowing.

